

VLSI LABORATORY EXPERIMENT

[By Sanuj Kulshrestha, 2017UEC2053, Group 2, ECE 1, Semester 6]

AIM

Simulate following using pass transmission logic

- Dynamic D-Latch
- Dynamic D Flip Flop
- Static D-Latch
- Static D Flip Flop

(I) For easy coding, making a SUBCKT of CMOS NOT Gate and WEAK CMOS NOT GATE. It will be included in all four netlists of this experiment.

```
*Following is circuit implementation of CMOS NOT GATE
* 1 - Vdd
* 2 - Input
* 3 - Output

*****
.SUBCKT CMOS_NOT 2 3 1

*Use following statement to vary model parameters
.include /Users/sanujkul/Documents/LTspice/libraries/180nm_model.txt


M1 3 2 1 1 P_180 w=5u l=.18u
M2 3 2 0 0 N_180 w=1.25u l=.18u

.ENDS CMOS_NOT
*****
.SUBCKT CMOS_WEAK_NOT 2 3 1

*Use following statement to vary model parameters
.include /Users/sanujkul/Documents/LTspice/libraries/180nm_model.txt

M1 3 2 1 1 P_180 w=0.36u l=.18u
M2 3 2 0 0 N_180 w=0.36u l=.18u

.ENDS CMOS_NOT
```

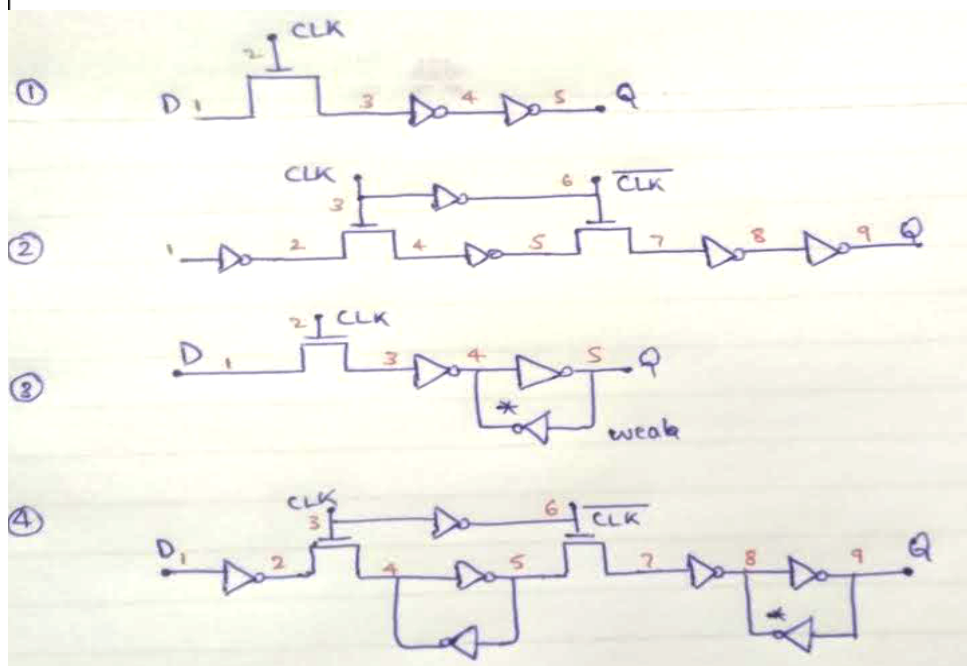

A. Dynamic D-Latch

```
.include /Users/sanujkul/Documents/LTspice/libraries/180nm_model.txt  
.include /Users/sanujkul/Documents/LTspice/Workspace/VLSI/libraries/CMOS-NOT.cir
```

```
M2 1 2 3 3 N_180 w=1.25u l=.18u
```

```
XNOT1 3 4 6 CMOS_NOT
```

```
XNOT2 4 5 6 CMOS_NOT
```

```
Vdd 6 0 DC 5v
```

```
C3 3 0 10p
```

```
C4 4 0 10p
```


```
C5 5 0 10p
```

```
Vd 1 0 PULSE(0 5v 1.75us 0.1fs 0.1fs 0.5us 1us)
```

```
Vclk 2 0 PULSE(0 5v 2us 0.1fs 0.1fs 2us 4us)
```

```
***** OUTPUT CODES *****
```

```
.TRAN 0 15us
```

 

B. Dynamic D Flip Flop

```
.include /Users/sanujkul/Documents/LTspice/libraries/180nm_model.txt  
.include /Users/sanujkul/Documents/LTspice/Workspace/VLSI/libraries/CMOS-NOT.cir
```

```
XNOT1 1 2 100 CMOS_NOT  
XNOT2 3 6 100 CMOS_NOT  
XNOT3 4 5 100 CMOS_NOT  
XNOT4 7 8 100 CMOS_NOT  
XNOT5 8 9 100 CMOS_NOT
```


```
M1 2 3 4 4 N_180 w=2.5u l=.18u  
M2 5 6 7 7 N_180 w=2.5u l=.18u
```

```
CL 9 0 5p  
C2 2 0 1p  
C4 4 0 1p  
C5 5 0 1p  
C6 6 0 1p  
C7 7 0 1p
```

```
Vdd 100 0 DC 5v
```

```
Vd 1 0 PULSE(0 5v 4us 0.1fs 0.1fs 0.5us 1us)  
Vclk 3 0 PULSE(0 5v 5.3us 0.1fs 0.1fs 2us 4us)
```
 
```
***** OUTPUT CODES *****  
.TRAN 0 15us
```



C. Static D-Latch

```
.include /Users/sanujkul/Documents/LTspice/libraries/180nm_model.txt
.include /Users/sanujkul/Documents/LTspice/Workspace/VLSI/libraries/
CMOS-NOT.cir
```

```
M2 1 2 3 3 N_180 w=1.25u l=.18u
```

```
XNOT1 3 4 6 CMOS_NOT
XNOT2 4 5 6 CMOS_NOT
XNOT3 5 4 6 CMOS_WEAK_NOT
```

```
Vdd 6 0 DC 5v
```

```
C3 3 0 10p
```

```
C4 4 0 10p
```


```
C5 5 0 10p
```

```
Vd 1 0 PULSE(0 5v 1.75us 0.1fs 0.1fs 0.5us 1us)
```

```
Vclk 2 0 PULSE(0 5v 2us 0.1fs 0.1fs 2us 4us)
```

```
**** OUTPUT CODES ****
```

```
.TRAN 0 15us
```

 

D. Static D Flip Flop

```
.include /Users/sanujkul/Documents/LTspice/libraries/180nm_model.txt
.include /Users/sanujkul/Documents/LTspice/Workspace/VLSI/libraries/CMOS-NOT.cir

XNOT1 1 2 100 CMOS_NOT
XNOT2 3 6 100 CMOS_NOT
XNOT3 4 5 100 CMOS_NOT
XNOT4 7 8 100 CMOS_NOT
XNOT5 8 9 100 CMOS_NOT

XNOT6 5 3 100 CMOS_WEAK_NOT
XNOT7 9 8 100 CMOS_WEAK_NOT

M1 2 3 4 4 N_180 w=2.5u l=.18u
M2 5 6 7 7 N_180 w=2.5u l=.18u

CL 9 0 5p
C2 2 0 1p
C4 4 0 1p
C5 5 0 1p
C6 6 0 1p
C7 7 0 1p

Vdd 100 0 DC 5v

Vd 1 0 PULSE(0 5v 4us 0.1fs 0.1fs 0.5us 1us)
Vclk 3 0 PULSE(0 5v 5.3us 0.1fs 0.1fs 2us 4us)

**** OUTPUT CODES ****
.TRAN 0 15us
```

